

CVM UNIVERSITY

M.Sc. (INSTRUMENTATION & CONTROL) Semester-I Examination-2021

Monday, 01st March – 2021

02:00 PM to 04:00 PM

101390107 INSTRUMENTATION OF PROCESSING CIRCUITS

Total Marks: 60

- Note: (1) Attempt all questions.
(2) Figures to the right indicate marks.

Q. 1 (a) Answer the following multiple choice questions. (08)

- (1) For an ideal comparator, what should be the value of the response time?
a) Zero b) Unity c) Infinite d) Unpredictable
- (2) Input Impedance of Practical Op-Amp is
a) Zero b) Very High c) Infinite d) Low
- (3) In Dead Zone Circuit, $V = +15\text{ V}$, $mR = 30\text{ kohm}$ and $R = 10\text{ kohm}$ so what is the value of reference voltage?
a) 5 V b) 15 V c) 20 V d) 10 V
- (4) What happens when the operating frequency of an op-amp increase?
a) Gain and phase shift of amplifier decreases
b) Phase shift between output and input signal decrease
c) Gain of the amplifier decrease
d) None of the mentioned
- (5) Flat- flat filter is also known as :
a) Bessel b) Chebyshev c) Cauer d) Butterworth
- (6) The cut off frequency occurs at attenuation of
a) 0 dB b) 3dB c) 10 dB d) 0.5 dB
- (7) Which amplifier provides twice output swing as that of LM380 amplifier?
a) Hybrid power amplifier
b) Monolithic power audio amplifier
c) Dual power amplifier
d) Bridge power audio amplifier
- (8) PLL first stage is:
a) VCO b) LPF c) Phase Detector d) None of the above

(b) Answer the following (Fill in the blanks and True or False) (08)

- (1) Zero crossing detector circuit plays a crucial role in conversion of input sine wave into a perfect _____ at its output.
- (2) Design a three channel inverting amplifier. The gains for each channel will be -10,-5 and -2 respectively and $R_1 = 100\text{ Kohm}$.
So value of $R_2 =$ _____ Kohm and $R_3 =$ _____ Kohm
- (3) The slew rate for a 741 is 0.5 V/microsecond. You can get an undistorted sine-wave output voltage of (a) 10 v peak, (b) 1 V peak At _____ and _____ maximum frequency respectively.
- (4) The common-mode gain is Very Low and ideally Zero.(True or False)
- (5) The minimum difference between two discrete values that can be distinguished by measuring device is _____.
- (6) The ratio between the modulating signal voltage and the carrier voltage is called modulating signal Frequency. (True or False)
- (7) The ratio of resonant frequency to bandwidth is called _____.

- (8) _____ filter produces a predictable phase shift characteristic in all frequencies.
- Q.2** Attempt **any six** of the following. **(12)**
- (1) Explain any one application of Zero-Crossing Detector.
 - (2) Give an account of Audio Mixer.
 - (3) Explain the Phase Shifter circuit.
 - (4) Explain DC Voltmeter.
 - (5) Explain Phase angle detection.
 - (6) Draw the Block diagram of Phase-Locked Loop.
 - (7) Write advantages of Active filter over Passive filter.
 - (8) Write application of NE/SE 566 and ICL8038.
- Q. 3** Describe any two practical application of Voltage level detector **(08)**
OR
- Q.3** Explain Multi-channel amplifier & Window Detector **(08)**
- Q. 4** Explain Instrumentation amplifier and its applications. **(08)**
OR
- Q. 4** With appropriate circuit and waveform explain AC to DC Converter. **(08)**
- Q. 5** Explain Sample & Hold Circuit. An S/H amplifier with an aperture time uncertainty of 50 ns is connected to an 8-bit ADC. Find the highest-frequency sine wave that can be digitized within an error of 1 LSB. **(08)**
OR
- Q. 5** Explain Amplitude Modulation & Demodulation Circuit and Frequency Shifting **(08)**
- Q. 6** Draw neat diagram of low pass filter circuit and frequency response curve. Write steps to design -60dB/ decade low pass Butterworth filter and determine the values of C1, C2 and R for a cut off frequency of 1 KHz where C3 = 0.01uF. **(08)**
OR
- Q. 6** Draw neat diagram of high pass filter circuit and frequency response curve for a 20 dB/decade slope and write the design procedure. If C = 0.002uF and f = 10KHz, Calculate R. **(08)**